

TED (21) 3033
(Revision-2021)

N22-2110220134A

Reg.No.....
Signature.....

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/MANAGEMENT/
COMMERCIAL PRACTICE, NOVEMBER - 2022**

FUNDAMENTALS OF ELECTRIC CIRCUITS

[Maximum marks: 75]

(Time: 3 Hours)

PART A

I. Answer all questions in one word or one sentence. Each question carries one mark.

(9 x 1 = 9 Marks)


		Module outcome	Cognitive level
1	Name any one energy source in an electric circuit.	M1.01	R
2	In Norton's equivalent circuit current source and resistance are connected in.....	M1.02	R
3	Convert $2 + j3$ into polar form	M2.01	U
4	Write the condition for resonance in an RLC series circuit	M2.04	R
5	Give the equation for reactive power in a single-phase AC circuit	M2.02	R
6	List any one method of solving parallel circuits.	M3.02	R
7	The reciprocal of impedance is called.....	M3.02	R
8	Name any one type of 3 phase connection	M4.02	R
9	Give the relation between phase value and line value of current in a 3 ϕ delta connected system	M4.02	U

PART B

II. Answer any eight questions from the following. Each question carries three marks.

(8 x 3 = 24 Marks)



		Module outcome	Cognitive level
1	Explain the steps to Thevenize a circuit	M1.03	U
2	State reciprocity theorem.	M1.02	R
3	Two phasors are given as $A = 4 + j3$ and $B = 5 + j6$. Calculate $\frac{A}{B}$ in rectangular and polar form.	M2.01	U
4	Explain the nature of current and voltage in a pure inductive circuit with a neat figure.	M2.01	U
5	Derive the expression for resonant frequency in a series RLC circuit.	M2.04	U
6	A 10Ω resistor, 15 mH inductor and $100\mu\text{F}$ capacitor are connected in parallel to a 200V, 50Hz, AC supply. Calculate the current in each branch.	M3.03	A


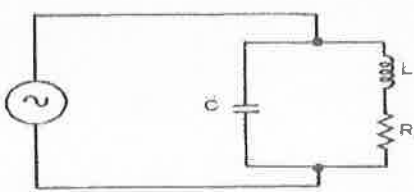
7	A parallel circuit is given in Fig.1. Given $R = 15\Omega$, $C = 2.5 \mu\text{F}$ and $L=260 \text{ mH}$. Calculate the resonant frequency.		
		M3.04	U
8	Draw the vector diagram of an AC circuit with R and L connected in parallel	M3.01	U
9	List any 3 advantages of 3 phase system.	M4.01	R
10	Write the expression of powers in a three-phase balanced system.	M4.04	R

PART C

Answer all questions. Each question carries seven marks

(6 x 7 = 42 Marks)

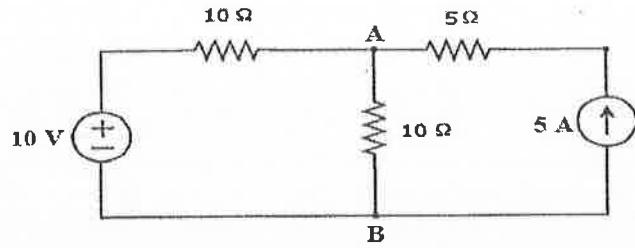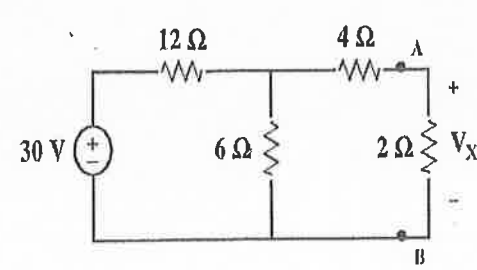		Module outcome	Cognitive level
III	Using superposition theorem calculate the current in the branch AB of the circuit shown below.		
		M1.04	A
OR			
IV	Calculate the voltage across 2Ω resistor using Thevenin's theorem		
		M1.04	A
V	Explain Norton's theorem along with the procedure to nortanize an electric circuit	M1.03	U
OR			
VI	Explain (i) Maximum power transfer theorem (ii) Superposition theorem	M1.03	U
VII	A resistor of 10Ω , is connected in series with a 0.2H inductor, across a 230V , 50Hz supply. Calculate (i) current (ii) voltage across each component (iii) the power dissipated.	M2.03	A

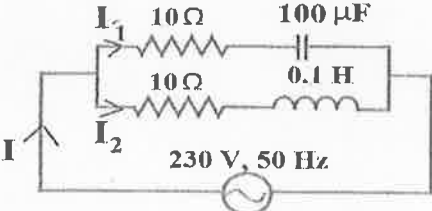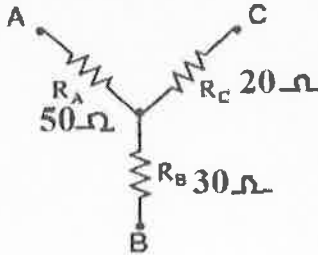VIII	<p style="text-align: center;">OR</p> <p>An impedance of $(8-j6)\Omega$ is connected to a voltage source of $(150 + j120)$ Volts. Calculate the current taken from the supply and power factor.</p>	M2.03	A
IX	<p>Two impedances $Z_1 = (10 + j5)\Omega$ and $Z_2 = (25 - j10)\Omega$ are connected in parallel across a 100 V, 50Hz AC source. Calculate the total current and power factor using admittance method.</p>	M3.03	A
X	<p style="text-align: center;">OR</p> <p>Draw the vector diagram for the following network.</p> 	M3.03	A
XI	<p>With the help of a vector diagram derive the relation between line voltage and phase voltage in a star connected system.</p> <p style="text-align: center;">OR</p>	M4.02	U
XII	<p>Write any 5 comparisons between a three-phase star and delta connected system.</p>	M4.02	U
XIII	<p>Three coils each with a resistance of 45Ω and inductance 0.2 H are connected in delta to a 415 V, 50 Hz, 3 phase supply. Calculate the current in each coil and total power absorbed.</p> <p style="text-align: center;">OR</p>	M4.04	A
XIV	<p>Draw the equivalent delta connected network for the given star connected network</p> 	M4.03	A
